

# Lab 7 Preliminary Report

**Labwork 7**

**FSM Design**

15.12.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

- **Gates**

- 5 x 74 LS/HC 11 Triple 3-input AND gate
- 3 x 74 LS/HC 32 Quad 2-input OR gate
- 1 x 74 LS/HC 74 ON Semiconductor- Dual D Flip-Flop
- 1 x 74 LS/HC 163 NXP Semiconductors - Presentable synchronous 4-bit binary counter

- **Objective**

In this week's lab experiment we are assigned to implement a Finite State Machine with various integrated circuit on the breadboard. I am going to implement a setup, a game of flipping coins, with FSM. Doing so I am going to use AND gates, OR gates, D Flip-Flop and for the input a synchronous 4-bit binary counter for my implementation.

-

- **Design Specification Plan**

- I am going to implement a game, in which player will have two coins and s/he will flip two coins at the same time. If a head of the coin comes its worth is '1' point, if tail of the coin comes it is '0' points. The aim of the game is collecting 4 points. Player can earn 0-point, 1-point or max 2-points at an attempt. Number of the attempts are not important, only thing important is collecting 4 points.

- **Proposed Design Methodology**

- I started my design from state diagram, in which I have 4 states. States are state1 is 0-point, state2 is 1-point, state3 is 2-points and last state, state4 is 3-points. F is the first coin and S is the second coin.

# Lab 7 Preliminary Report

## Labwork 7


### FSM Design

15.12.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

## State diagram

 

- After drawing state diagram, I draw my Karnaugh maps to find  $D_1$  and  $D_0$ , the inputs of the D Flip-Flop, which is determined by outputs of the D Flip-Flop  $Q_1$  and  $Q_0$  and inputs F and S.

		FS			
		00	01	11	10
$Q_1 Q_0$	00	0	0	1	0
	01	0	1	1	1
	11	1	0	0	0
	10	1	1	0	1

		FS			
		00	01	11	10
$Q_1 Q_0$	00	0	1	0	1
	01	1	0	1	0
	11	1	0	1	0
	10	0	1	0	1

- According to my K- maps I find my SOPs of  $D_1$  and  $D_0$ .

$$D_1 = \overline{Q_1} \cdot F \cdot S + \overline{Q_1} \cdot Q_0 \cdot F + \overline{Q_1} \cdot Q_0 \cdot S + Q_1 \cdot \overline{F} \cdot \overline{S} + Q_1 \cdot \overline{Q_0} \cdot \overline{F} + Q_1 \cdot \overline{Q_0} \cdot \overline{S}$$

$$D_0 = \overline{Q_0} \cdot \overline{F} \cdot S + \overline{Q_0} \cdot F \cdot \overline{S} + Q_0 \cdot \overline{F} \cdot \overline{S} + Q_1 \cdot F \cdot S$$

# Lab 7 Preliminary Report

## Labwork 7


### FSM Design

15.12.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

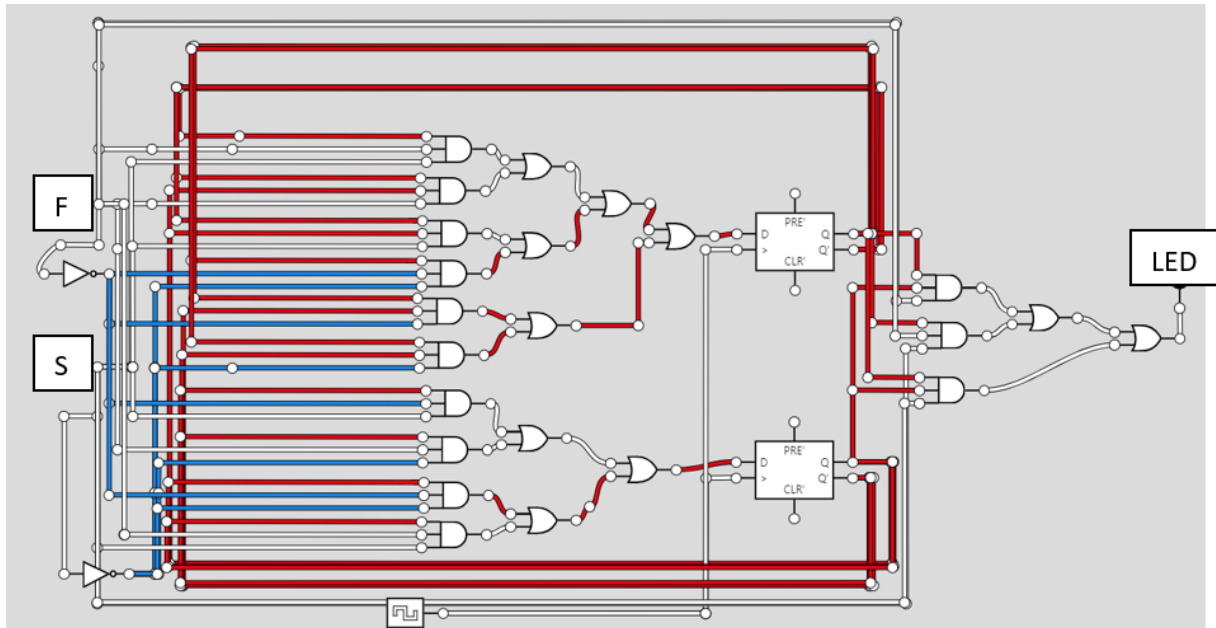- Looking for these equations I draw my schematic design of the desired circuit.



- Looking at y schematic I find the IC that I need and how many of them I will in my implementation.

