

- The Design Methodology**

In my case output is entrance to bank vault at the gas station and inputs are S(supervisor), C(cashier) and R(rookie). Only the S(supervisor) has access the bank vault so if someone else wants to get in the vault they must be together with the S(supervisor). Also, R(rookie) always must be with the C(cashier) to be monitored. If R(rookie) is in the vault, then C(cashier) must be in the vault as well as the supervisor. To provide these conditions first I designed truth table accordingly. Then I produce the logic expression from the sum of products method.

- Results:**

S	C	R	H(S,C,R)	Minterms
0	0	0	0	m_0
0	0	1	0	m_1
0	1	0	0	m_2
0	1	1	0	m_3
1	0	0	1	m_4
1	0	1	0	m_5
1	1	0	1	m_6
1	1	1	1	m_7

Truth Table

$$\text{Sum of Products(minterms)} = \sum m(4,6,7) = m_4 + m_6 + m_7 = H(S, C, R)$$

$$H(S, C, R) = S \cdot \bar{C} \cdot \bar{R} + S \cdot C \cdot \bar{R} + S \cdot C \cdot R$$


$$= S \cdot \bar{C} \cdot \bar{R} + S \cdot C \cdot (\bar{R} + R)$$

$$= S \cdot \bar{C} \cdot \bar{R} + S \cdot C$$

$$= S \cdot (\bar{C} \cdot \bar{R} + C)$$


$$H(S, C, R) = S \cdot (\bar{C} \cdot \bar{R} + C)$$

Logic Schematic Diagram

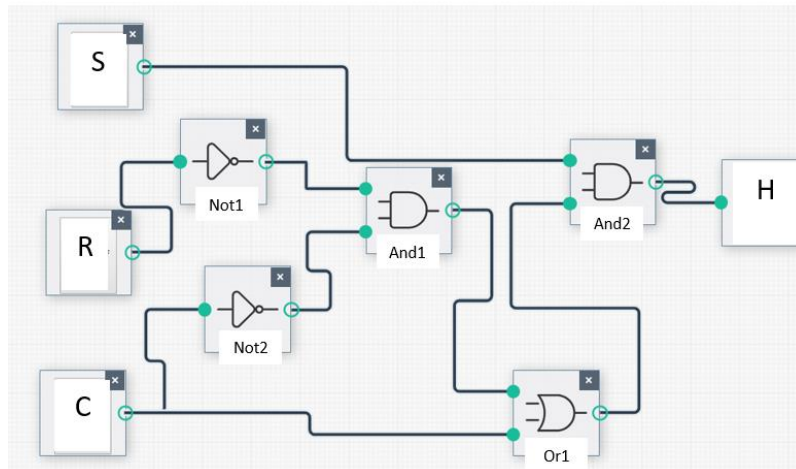


- Circuit Diagram:

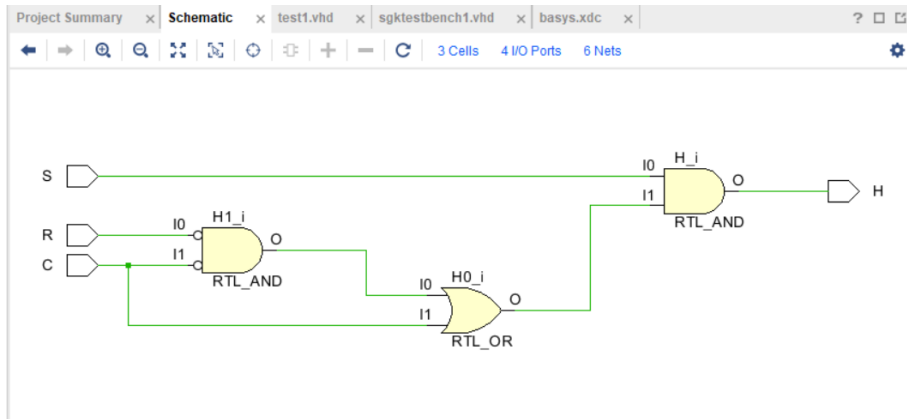Program uses bubble to bubble logic to show the diagram of my logic expression. Displayed diagram a bit different but truth table is same with mien.



- Simulation:

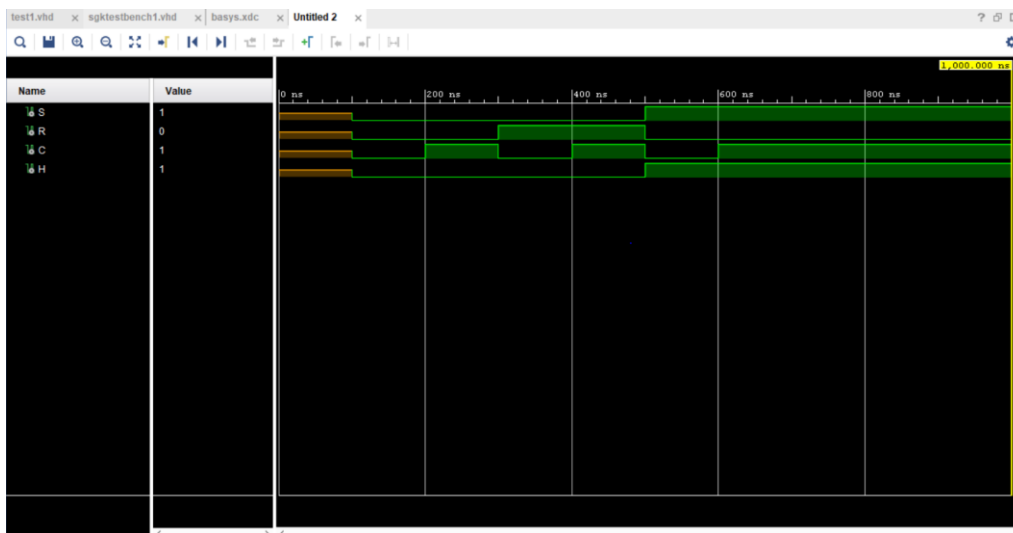I entered 8 different case and they are all matching with my truth table.



These are photos of the all possible 8 scenerios:



Case8



Case7




Case6



Case5




Case4

 

Case3



Case2

 

Case1

- **Conclusion:**

After doing this lab, with help of the tutorial that uploaded to the Moodle I learnt how to use Vivado program such as adding design sources, simulation sources, adding constraints, how to write pin configuration, generating Bitstreams to use on Basys3 and most important thing I learnt is writing codes in VHDL code language. To conclude, with all of these I complete Lab02 assignment by myself.

- **Appendices :**

VHDL code:

- **Design sources:**

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

entity test1 is

```
    Port ( S : in STD_LOGIC;  
          R : in STD_LOGIC;  
          C : in STD_LOGIC;  
          H : out STD_LOGIC);
```

end test1;

architecture Behavioral of test1 is

begin

```
H <= S and ((not R and not C) or C);
```

end Behavioral;

- **Simulation sources:**

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

entity sgktestbench1 is

end sgktestbench1;

architecture Behavioral of sgktestbench1 is

component test1

```
Port ( S : in STD_LOGIC;
      R : in STD_LOGIC;
      C : in STD_LOGIC;
      H : out STD_LOGIC);
end component;
SIGNAL S : STD_LOGIC;
SIGNAL R : STD_LOGIC;
SIGNAL C : STD_LOGIC;
SIGNAL H : STD_LOGIC;
BEGIN
UUT: test1 PORT MAP(
S => S,
R => R,
C => C,
H => H
);
testBench1 : PROCESS
BEGIN
wait for 100 ns;
S<='0';
R<='0';
C<='0';
wait for 100 ns;
S<='0';
R<='0';
C<='1';
wait for 100 ns;
S<='0';
R<='1';
C<='0';
wait for 100 ns;
S<='0';
R<='1';
C<='1';
wait for 100 ns;
S<='1';
R<='0';
C<='0';
wait for 100 ns;
S<='1';
R<='0';
C<='1';
wait for 100 ns;
```

```
S<='1';
R<='1';
C<='0';
wait for 100 ns;
S<='1';
R<='1';
C<='1';

END PROCESS;
end Behavioral;
```

- **Constrains:**

```
set_property PACKAGE_PIN V17 [get_ports {S}]
  set_property IOSTANDARD LVCMOS33 [get_ports {S}]
set_property PACKAGE_PIN V16 [get_ports {R}]
  set_property IOSTANDARD LVCMOS33 [get_ports {R}]
set_property PACKAGE_PIN U16 [get_ports {H}]
  set_property IOSTANDARD LVCMOS33 [get_ports {H}]
set_property PACKAGE_PIN W16 [get_ports {C}]
  set_property IOSTANDARD LVCMOS33 [get_ports {C}]
connect_debug_port dbg_hub/clk [get_nets <clock_net_name>]
```