

Lab 4 Report

Labwork 4 Seven Segment Display

31.10.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

• Design Methodology

I establish this lab's purpose with the scenario that I used in Lab02. In the scenario there is a Supervisor (S1), Rookie(S2), Cashier(S3) and the goal is getting inside the bank vault. Only the supervisor has an access the bank vault so if someone else wants to get in the vault they must be together with the supervisor. Also, rookie always must be with the cashier in order to be monitored. If rookie is in the vault cashier must be in the vault as well as the supervisor. At the seven-segment display S1 S2 S3 L4 will be displayed with '1' s and '0' s according to their values which means if the value is 0 then LED_on = "0000001", if it is 1 then LED_on = "1001111".

- Differences from Preliminary:

- I added clock module and I am using it to display 4 different seven-segments at the same time on Basys3
- About Activator and LED_bin I changed the locations and the way I used them in my code.
- I added 4 LEDs to visualize inputs and outputs values.

• Results

K-MAP

		S3 S2			
S1	0	00	01	11	10
	1	0	0	1	1

Lab 4 Report

Labwork 4 Seven Segment Display

31.10.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

Truth Table

S	C	R	H(S,C,R)	Minterms
0	0	0	0	m_0
0	0	1	0	m_1
0	1	0	0	m_2
0	1	1	0	m_3
1	0	0	1	m_4
1	0	1	0	m_5
1	1	0	1	m_6
1	1	1	1	m_7

Sum of products(minterms) = $\sum m(4,6,7) = m_4 + m_6 + m_7 = H(S, C, R)$

$$H(S, C, R) = S \cdot \bar{C} \cdot \bar{R} + S \cdot C \cdot \bar{R} + S \cdot C \cdot R$$


$$= S \cdot \bar{C} \cdot \bar{R} + S \cdot C \cdot (\bar{R} + R)$$

$$= S \cdot \bar{C} \cdot \bar{R} + S \cdot C$$

$$= S \cdot (\bar{C} \cdot \bar{R} + C)$$

$$H(S, C, R) = S \cdot (\bar{C} \cdot \bar{R} + C)$$

Logic Schematic Diagram

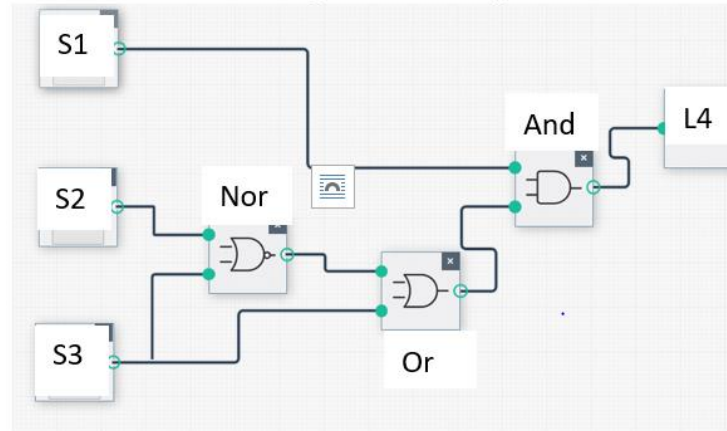

Lab 4 Report

Labwork 4


Seven Segment Display

31.10.2018


Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

Schematic

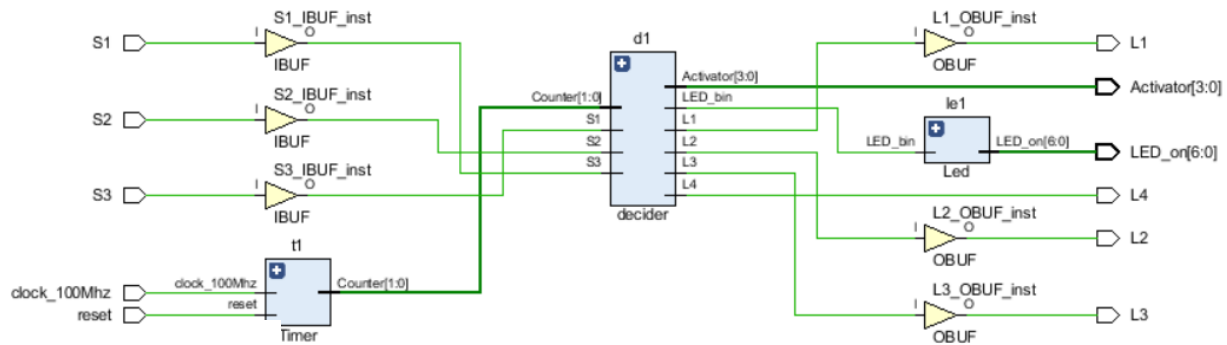

Test bench of decider

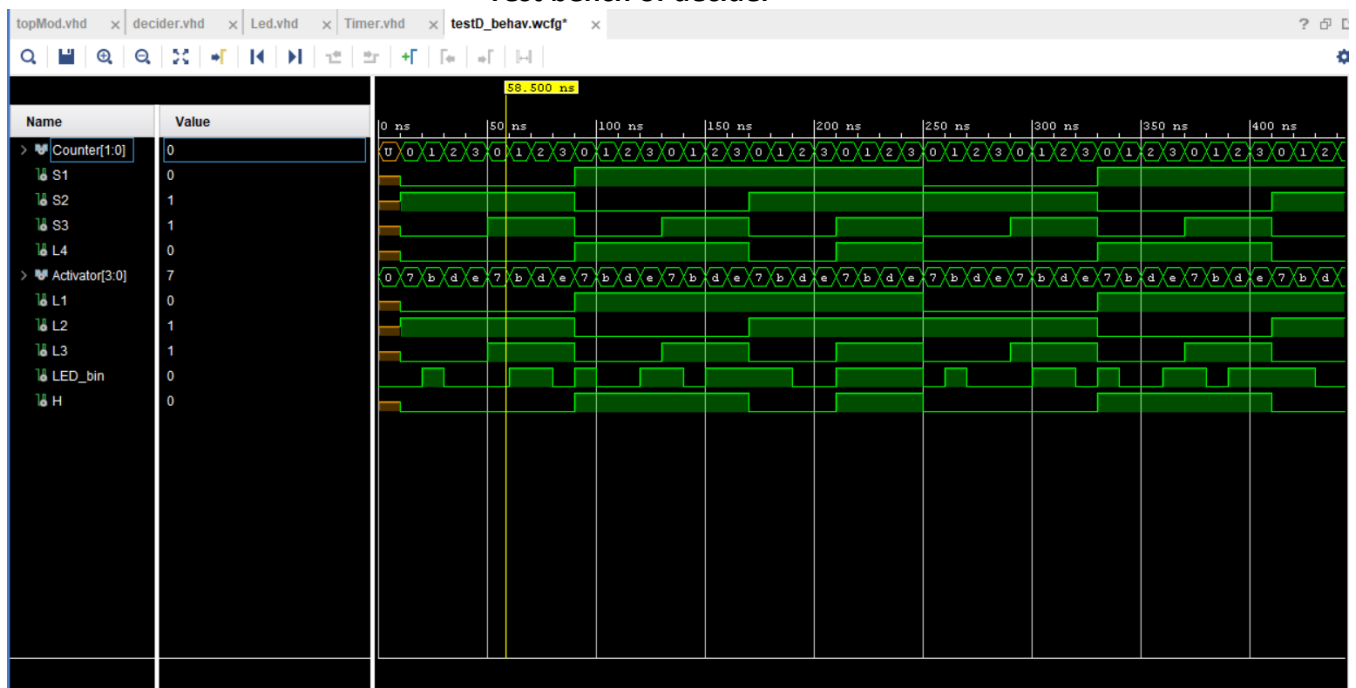


Lab 4 Report

Labwork 4 Seven Segment Display


31.10.2018

Şevki Gavrem Kulkuloğlu


21601793 EE 102 -2

 

S1:0 S2:0 S3:0 L4:0

 

S1:0 S2:0 S3:1 L4:0

 

S1:0 S2:1 S3:0 L4:0


Lab 4 Report

Labwork 4 Seven Segment Display


31.10.2018

Şevki Gavrem Kulkuloğlu


21601793 EE 102 -2

 

S1:0 S2:1 S3:1 L4:0

 

S1:1 S2:0 S3:0 L4:1

 

S1:1 S2:0 S3:1 L4:1

Lab 4 Report


Labwork 4

Seven Segment Display


31.10.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

 

S1:1 S2:1 S3:0 L4:0

 

S1:1 S2:1 S3:1 L4:1

Lab 4 Report

Labwork 4
Seven Segment Display

31.10.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

• Conclusion

I have learnt the differences between variable types like in, out, inout, signals... and places where can we use them, or which one must use. I have faced with some errors like “usf-xsim-62 'elaborate' step failed with error(s)” and I learnt to track the log files and find the errors. I have learnt whether I included all possible values I should also add “others” case in cases. I have learnt how to use top and sub modules and how to write test bench in better way. I also have learnt how to use seven-segment display in which how to display numbers and letters, how to order them and showing four seven segments at the same time using clock on the Basys3.

• Appendices

- VHDL:

TopModule:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity topMod is
    Port ( clock_100Mhz : in STD_LOGIC;
          reset : in STD_LOGIC;
          S3,S2,S1 : in STD_LOGIC;
          L4,L3,L2,L1 : out STD_LOGIC;
          Activator : out STD_LOGIC_VECTOR (3 downto 0);
          LED_on : out STD_LOGIC_VECTOR (6 downto 0));
end topMod;
```

```
architecture Behavioral of topMod is
    signal Counter_temp: std_logic_vector(1 downto 0);
    signal BIN_LED: std_logic;
```

```
component decider is
    PORT
    (
        Counter : in std_logic_vector(1 downto 0);
        S3,S2,S1 : in STD_LOGIC;
        Activator : out std_logic_vector(3 downto 0);
        L4,L3,L2,L1 : out STD_LOGIC;
        LED_bin : out STD_LOGIC);
```

Lab 4 Report

Labwork 4 Seven Segment Display

31.10.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

```
end component;
```

```
component Led is
```

```
PORT
```

```
(LED_bin : in STD_LOGIC;
```

```
LED_on : out STD_LOGIC_VECTOR (6 downto 0));
```

```
end component;
```

```
component Timer is
```

```
PORT
```

```
(clock_100Mhz : in STD_LOGIC;
```

```
reset : in STD_LOGIC;
```

```
Counter: out std_logic_vector(1 downto 0));
```

```
end component;
```

```
begin
```

```
d1 : decider PORT MAP (Counter_temp,S1,S2,S3,Activator,L4,L3,L2,L1,BIN_LED);
```

```
le1: Led PORT MAP (BIN_LED,LED_on);
```

```
t1 : Timer PORT MAP ( clock_100Mhz,reset,Counter_temp);
```

```
end Behavioral;
```

Decider module:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity decider is
```

```
Port ( Counter : in std_logic_vector(1 downto 0);
```

```
S1 : in STD_LOGIC;
```

```
S2 : in STD_LOGIC;
```

```
S3 : in STD_LOGIC;
```

```
Activator : out std_logic_vector(3 downto 0);
```

```
L1 : out STD_LOGIC;
```

```
L2 : out STD_LOGIC;
```

```
L3 : out STD_LOGIC;
```

```
L4 : out STD_LOGIC;
```

```
LED_bin : out STD_LOGIC);
```

```
end decider;
```

```
architecture Behavioral of decider is
```

```
signal H: STD_LOGIC;
```

```
begin
```

```
H <= S1 and (( not S2 and not S3) or S3);
```


Lab 4 Report

Labwork 4

Seven Segment Display

31.10.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

```
L1 <= S1;  
L2 <= S2;  
L3 <= S3;  
L4 <= H;
```

```
process(Counter,S1)  
begin  
  case Counter is  
    when "00" =>  
      Activator <= "0111";  
      LED_bin <= S1;  
    when "01" =>  
      Activator <= "1011";  
      LED_bin <= S2;  
    when "10" =>  
      Activator <= "1101";  
      LED_bin <= S3;  
    when "11" =>  
      Activator <= "1110";  
      LED_bin <= H;  
    when others =>  
      Activator <= "0000";  
      LED_bin <= '0';  
  end case;  
end process;
```

end Behavioral;

Led Module:

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity Led is  
  Port ( LED_bin : in STD_LOGIC;  
        LED_on : out STD_LOGIC_VECTOR (6 downto 0));  
end Led;
```

architecture Behavioral of Led is

begin

```
process(LED_bin)  
begin  
  case LED_bin is  
    when '0' => LED_on <= "0000001";
```

Lab 4 Report

Labwork 4

Seven Segment Display

31.10.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

```
when '1' => LED_on <= "1001111";
when others => LED_on <= "0000001";

end case;
end process;

end Behavioral;
```

Timer Module:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_unsigned.all;

entity Timer is
    Port ( clock_100Mhz : in STD_LOGIC;
          reset : in STD_LOGIC;
          Counter: out std_logic_vector(1 downto 0));
end Timer;

architecture Behavioral of Timer is
    signal refresh_counter: STD_LOGIC_VECTOR (19 downto 0);
begin

    process(clock_100Mhz,reset)
    begin
        if(reset='1') then
            refresh_counter <= (others => '0');
        elsif(rising_edge(clock_100Mhz)) then
            refresh_counter <= refresh_counter + 1;
        end if;
    end process;
    Counter <= refresh_counter(19 downto 18);

end Behavioral;
```

TESTBENCHES:

TESTD:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity testD is
end testD;
```

Lab 4 Report

Labwork 4 Seven Segment Display

31.10.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

architecture Behavioral of testD is

component decider is

```
Port ( Counter : in std_logic_vector(1 downto 0);
      S1 : in STD_LOGIC;
      S2 : in STD_LOGIC;
      S3 : in STD_LOGIC;
      Activator : out std_logic_vector(3 downto 0);
      L1 : out STD_LOGIC;
      L2 : out STD_LOGIC;
      L3 : out STD_LOGIC;
      L4:out STD_LOGIC;
      LED_bin : out STD_LOGIC
    );
end component;
```

```
signal Counter : std_logic_vector(1 downto 0);
signal S1 : STD_LOGIC;
signal S2 : STD_LOGIC;
signal S3 : STD_LOGIC;
signal L4 : STD_LOGIC;
signal Activator : std_logic_vector(3 downto 0) := "0000";
signal L1 : STD_LOGIC;
signal L2 : STD_LOGIC;
signal L3 : STD_LOGIC;
signal LED_bin : STD_LOGIC := '0';
```

begin

```
UUT: decider PORT MAP(
Counter => Counter,
S1 => S1,
S2 => S2,
S3 => S3,
L4 => L4,
Activator => Activator,
L1 => L1,
L2 => L2,
L3 => L3,
LED_bin => LED_bin
--Activator => Activator
);
```

Bench1: PROCESS

begin

```
--wait for 100 ns;
--Counter <= "00";
--S1 <= '0';
```

Lab 4 Report

Labwork 4

Seven Segment Display

31.10.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

```
--S2 <= '0';
--S3 <= '0';
--wait for 100 ns;
--Counter <= "01";
--S1 <= '0';
--S2 <= '0';
--S3 <= '0';
--wait for 100 ns;
--Counter <= "10";
--S1 <= '0';
--S2 <= '0';
--S3 <= '0';wait for 100 ns;
--Counter <= "10";
--S1 <= '0';
--S2 <= '0';
--S3 <= '0';
```

```
-----
--wait for 100 ns;
--Counter <= "00";
--S1 <= '0';
--S2 <= '0';
--S3 <= '1';
--wait for 100 ns;
--Counter <= "01";
--S1 <= '0';
--S2 <= '0';
--S3 <= '1';
--wait for 100 ns;
--Counter <= "10";
--S1 <= '0';
--S2 <= '0';
--S3 <= '1';
--wait for 100 ns;
--Counter <= "11";
--S1 <= '0';
--S2 <= '0';
--S3 <= '1';
```

```
-----
wait for 10 ns;
Counter <= "00";
S1 <= '0';
S2 <= '1';
S3 <= '0';
wait for 10 ns;
Counter <= "01";
```

Lab 4 Report

Labwork 4

Seven Segment Display

31.10.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

```
S1 <= '0';
S2 <= '1';
S3 <= '0';
wait for 10 ns;
Counter <= "10";
S1 <= '0';
S2 <= '1';
S3 <= '0';
wait for 10 ns;
Counter <= "11";
S1 <= '0';
S2 <= '1';
S3 <= '0';
```

```
-----
wait for 10 ns;
Counter <= "00";
S1 <= '0';
S2 <= '1';
S3 <= '1';
wait for 10 ns;
Counter <= "01";
S1 <= '0';
S2 <= '1';
S3 <= '1';
wait for 10 ns;
Counter <= "10";
S1 <= '0';
S2 <= '1';
S3 <= '1';
wait for 10 ns;
Counter <= "11";
S1 <= '0';
S2 <= '1';
S3 <= '1';
```

```
-----
wait for 10 ns;
Counter <= "00";
S1 <= '1';
S2 <= '0';
S3 <= '0';
wait for 10 ns;
Counter <= "01";
S1 <= '1';
S2 <= '0';
S3 <= '0';
```


Lab 4 Report

Labwork 4

Seven Segment Display

31.10.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

```
wait for 10 ns;
Counter <= "10";
S1 <= '1';
S2 <= '0';
S3 <= '0';
wait for 10 ns;
Counter <= "11";
S1 <= '1';
S2 <= '0';
S3 <= '0';
```

```
-----
wait for 10 ns;
Counter <= "00";
S1 <= '1';
S2 <= '0';
S3 <= '1';
wait for 10 ns;
Counter <= "01";
S1 <= '1';
S2 <= '0';
S3 <= '1';
wait for 10 ns;
Counter <= "10";
S1 <= '1';
S2 <= '0';
S3 <= '1';
wait for 10 ns;
Counter <= "11";
S1 <= '1';
S2 <= '0';
S3 <= '1';
```

```
-----
wait for 10 ns;
Counter <= "00";
S1 <= '1';
S2 <= '1';
S3 <= '0';
wait for 10 ns;
Counter <= "01";
S1 <= '1';
S2 <= '1';
S3 <= '0';
wait for 10 ns;
Counter <= "10";
S1 <= '1';
S2 <= '1';
```

Lab 4 Report

Labwork 4 Seven Segment Display

31.10.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

```
S3 <= '0';
wait for 10 ns;
Counter <= "11";
S1 <= '1';
S2 <= '1';
S3 <= '0';
```

```
-----
wait for 10 ns;
Counter <= "00";
S1 <= '1';
S2 <= '1';
S3 <= '1';
wait for 10 ns;
Counter <= "01";
S1 <= '1';
S2 <= '1';
S3 <= '1';
wait for 10 ns;
Counter <= "10";
S1 <= '1';
S2 <= '1';
S3 <= '1';
wait for 10 ns;
Counter <= "11";
S1 <= '1';
S2 <= '1';
S3 <= '1';
End process;
end Behavioral;
```

```
TESTLED:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity testLed is
end testLed;
```

```
architecture Behavioral of testLed is
component Led is
```

```
    Port (
        LED_bin : in STD_LOGIC;
        LED_on : out STD_LOGIC_VECTOR (6 downto 0));
```

```
end component;
```

```
signal LED_bin : STD_LOGIC;
```

```
signal LED_on : STD_LOGIC_VECTOR (6 downto 0) := b"0000000" ;
```

```
begin
```

```
UUT: Led PORT MAP(
```

Lab 4 Report

Labwork 4 Seven Segment Display

31.10.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

```
LED_bin => LED_bin,  
LED_on=> LED_on);
```

```
Bench1: PROCESS
```

```
begin  
wait for 10 ns;  
LED_bin<='0';  
wait for 10 ns;  
LED_bin<='1';  
end PROCESS;  
end Behavioral;
```

```
TEST_TIME:
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
entity testTime is  
end testTime;  
architecture Behavioral of testTime is  
component Timer is  
Port ( clock_100Mhz : in STD_LOGIC;  
reset : in STD_LOGIC;  
Counter: out std_logic_vector(1 downto 0));  
end component;  
signal clock_100Mhz : STD_LOGIC;  
signal reset : STD_LOGIC;  
signal Counter: std_logic_vector(1 downto 0);  
begin  
UUT: Timer PORT MAP(  
clock_100Mhz => clock_100Mhz,  
reset => reset,  
Counter => Counter  
);
```

```
Bench2: PROCESS
```

```
begin  
wait for 50 ns;  
clock_100Mhz <= '0';  
reset <= '0';  
wait for 50 ns;  
clock_100Mhz <= '0';  
reset <= '1';  
wait for 50 ns;  
clock_100Mhz <= '1';  
reset <= '0';  
wait for 50 ns;  
clock_100Mhz <= '1';
```

Lab 4 Report

Labwork 4

Seven Segment Display

31.10.2018

Şevki Gavrem Kulkuloğlu

21601793 EE 102 -2

```
reset <= '1';  
wait for 50 ns;  
clock_100Mhz <= '0';  
reset <= '0';  
end PROCESS;  
end Behavioral;
```